

V-089

Roll No. ~~21111111~~

Total Printed Pages : 3

05BEC102

B.TECH (ELEC. & COMM. ENGG.)

V-SEM Examination, Dec.-2016

SUB: LINEAR INTEGRATED CIRCUITS

Time : 3 Hours]

[Total Marks 60

Use of following supporting material is permitted during examination.

1. \_\_\_\_\_ Nil \_\_\_\_\_ Nil \_\_\_\_\_

Note: 1. Attempt any five questions selecting one question from each unit.

2. Each question carry equal marks.

### UNIT-I

1. Define 'unbalanced output'. Derive the expressions for DC and AC analysis of dual input balanced output differential amplifier.

OR

05BEC102

1

Contd...

LTC

1. What is **adder**? Explain non-inverting amplifier with expressions and diagrams.

**UNIT-II**

2. Define an oscillator. What are the two requirements for oscillations? Describe the principle and frequency response of integrator.

**OR**

2. Explain following –(any two)

- i) Differentiator
- ii) Square wave generator
- iii) wein bridge oscillator

**UNIT-III**

3. Explain low pass filter with first order and second order low pass Butterworth filter.

**OR**

3. What is filter? Explain wide and narrow band pass filter.

05BEC102

2

Contd...

4. Explain operation of PLL with the help of block diagram. Also give brief description of each block.

**UNIT-IV**

**OR**

4. What is a phase locked loop? Derive the expression for lock range in PLL.

**UNIT-V**

5. Explain the 555 timer as astable and monostable multivibrators.

**OR**

5. Write short notes on-

- i) Zero crossing detector
- ii) Schmitt trigger
- iii) Multiplier.

05BEC102

3